

# Advanced Topology - Marx Modulators

**Pulsed Power Engineering  
Texas A&M University  
February 7-18, 2022**

Craig Burkhart, Tony Beukers and Mark Kemp



SLAC National Accelerator Laboratory

David E. Anderson, G. Chris Pappas and Jared Walden



Oak Ridge National Laboratory

Will Waldron




Berkeley Lab



**U.S. Particle Accelerator School**  
Education in Beam Physics and Accelerator Technology
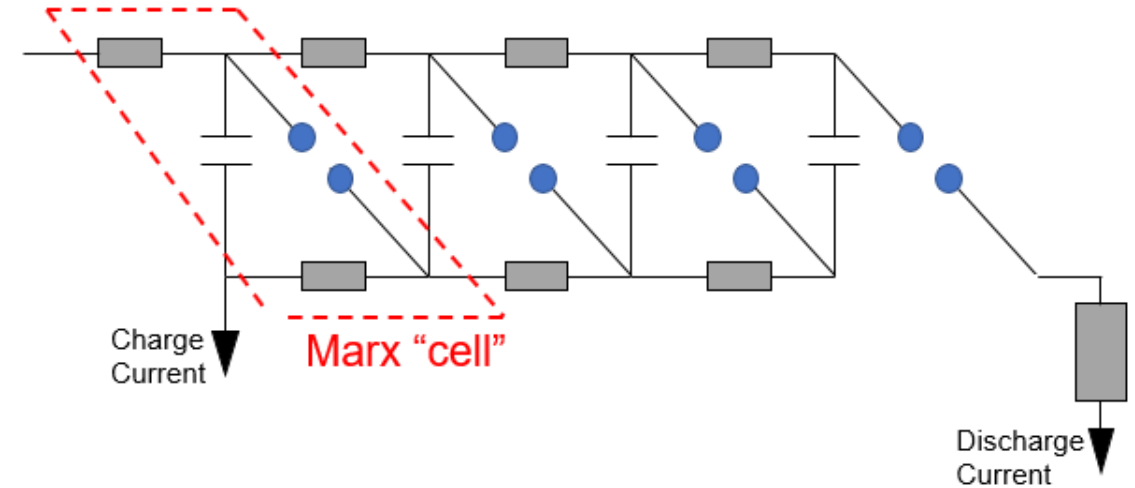
# Basic Marx Generator


- Concept first proposed by Erwin Marx in 1925
  - Charge capacitors in parallel
    - Maximum voltage:  $V$
    - Total capacitance:  $C \cdot N$
  - Discharge them in series
    - Maximum voltage:  $N \cdot V$
    - Total capacitance:  $C/N$
- Applicable over wide range of parameters
  - $\text{Sub-}\mu\text{s} < \text{pulse length} < \text{multi-}\mu\text{s}$
  - $\sim 0.1 \text{ MV} < \text{output voltage} < \text{over } 10 \text{ MV}$
- Simplifies voltage insulation and reduces switch voltage by factor of  $N$  (up to  $\sim 100$ )
  - Relatively low voltage on long time scales (charging)
  - High voltage only present while being delivered to load



- Historically, switched with spark gaps. Triggering the first spark gap leads the other spark gaps to self commute.
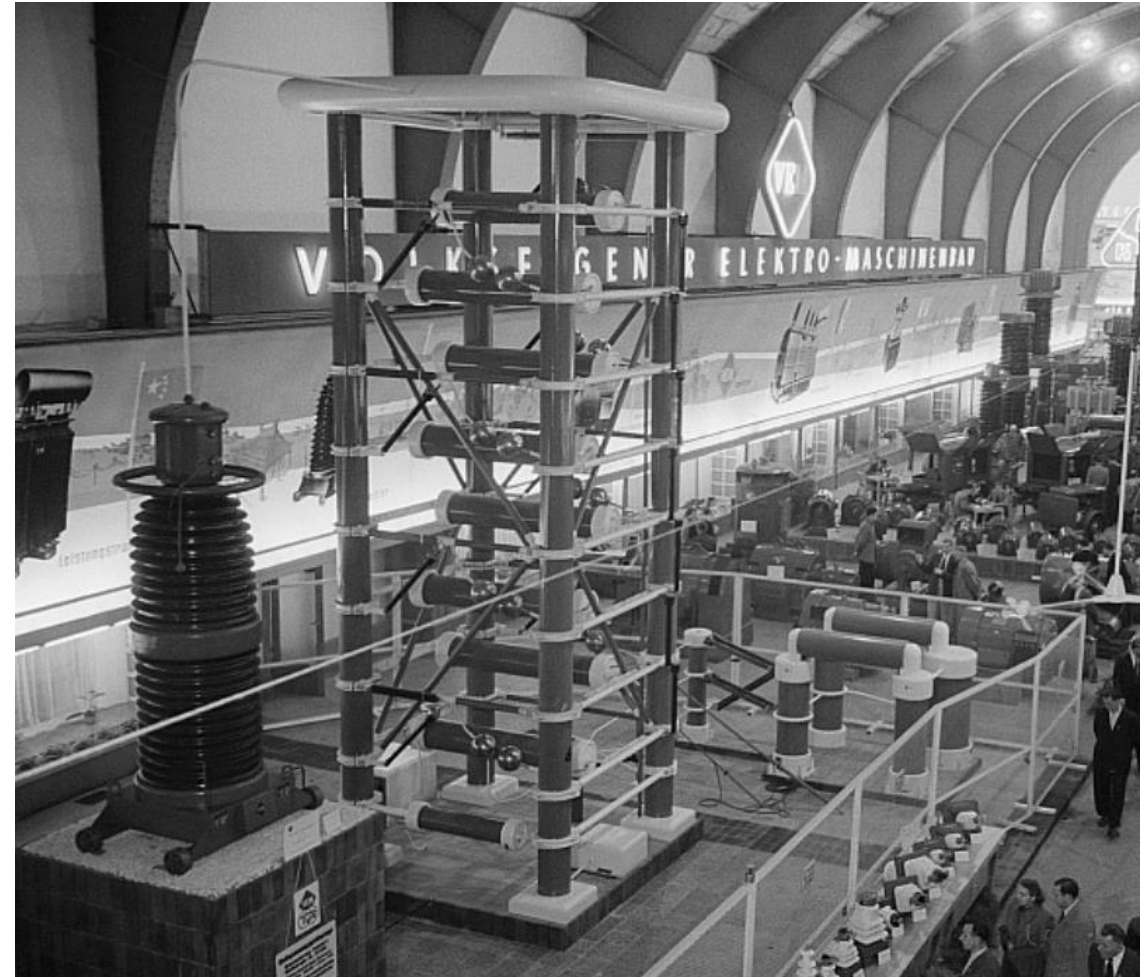
# Basic Marx Generator

- Necessitates isolation elements between stages (R or L historically) that can hold off V
- Waveform subject to distortion
  - Reduced output voltage
  - Slow risetime
  - Impaired stage triggering
  - Due to parasitic circuit elements
    - Capacitance
      - Stage-to-stage
      - Stage-to-ground
    - Inductance
      - Switch
      - Capacitor
      - Leads/layout



Autumn exhibition of State-Owned Electrical Engineering Enterprises (VEM) at Leipzig, East Germany, 1954. Marx generator to test electric utility power transmission equipment. Deutsche Fotothek.

# Basic Marx Generator

- Total output voltage
  - Without parasitics, output voltage is number of stages times the charging voltage
- Total energy storage
  - The total capacitance is the number of stages times the stage capacitance

$$E_{total} = \frac{1}{2} N_{stage} * C_{stage} * V_{charge}^2$$

- Equivalently, the total energy is the series capacitance times the output voltage

$$E_{total} = \frac{1}{2} \frac{C_{stage}}{N_{stage}} * (V_{charge} * N_{stage})^2$$


# Basic Marx Generator

- The output shape depends on parasitics, the nature of the switch timing, and the load impedance. Most simply, the erected Marx is a capacitance discharging into a resistance
- For many accelerator applications, the output pulse must be truncated. Therefore, opening switches are required. These also prevent excess energy transfer to the load during a fault



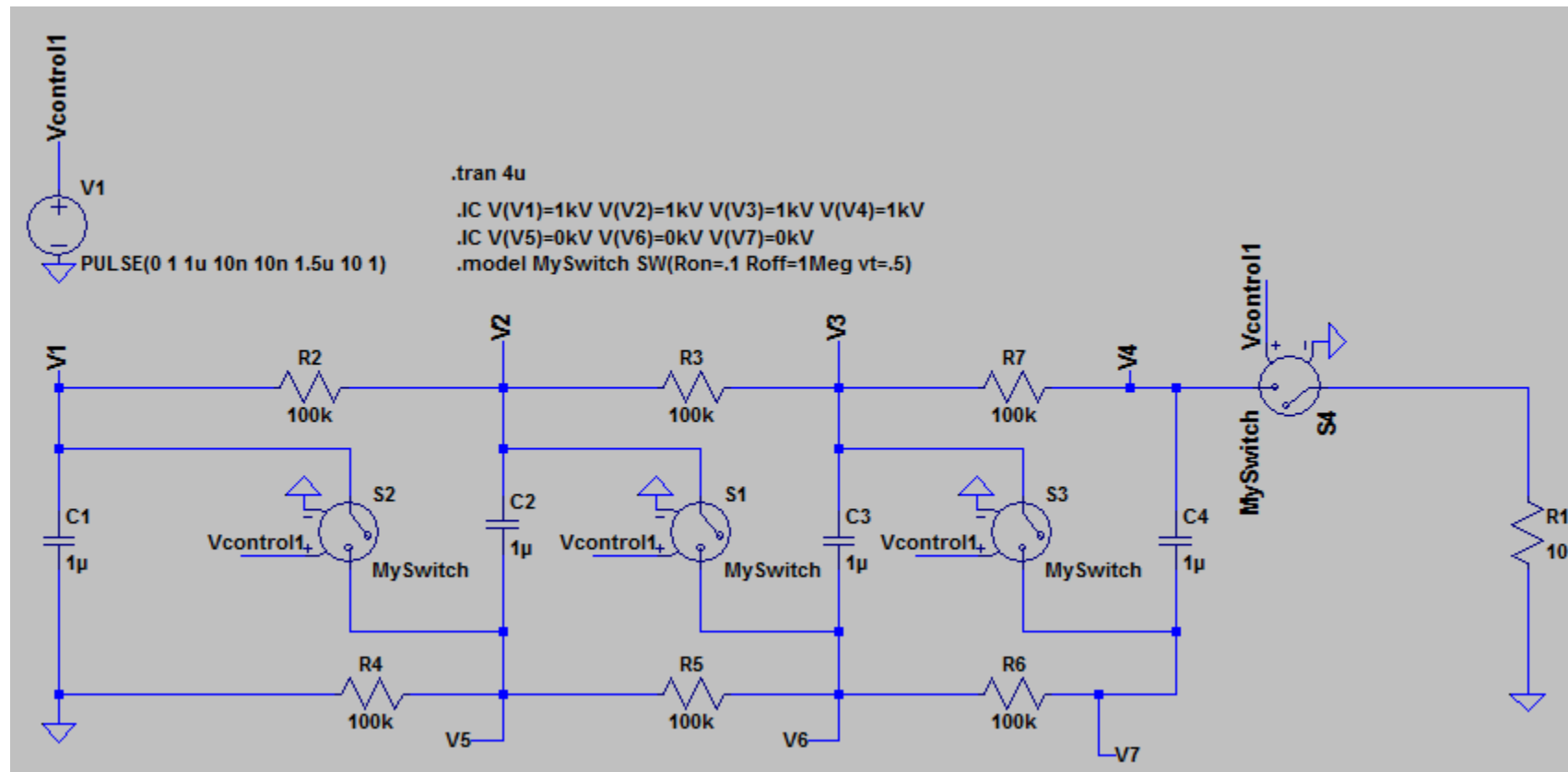
# Marx-parasitics

- Start with a simulation of an “ideal” 4 stage Marx
- Each stage is 1  $\mu\text{F}$  and charged to 1kV
- Load is a 10 Ohm resistor
- Switches turn on for 1.5  $\mu\text{s}$ , then turn off



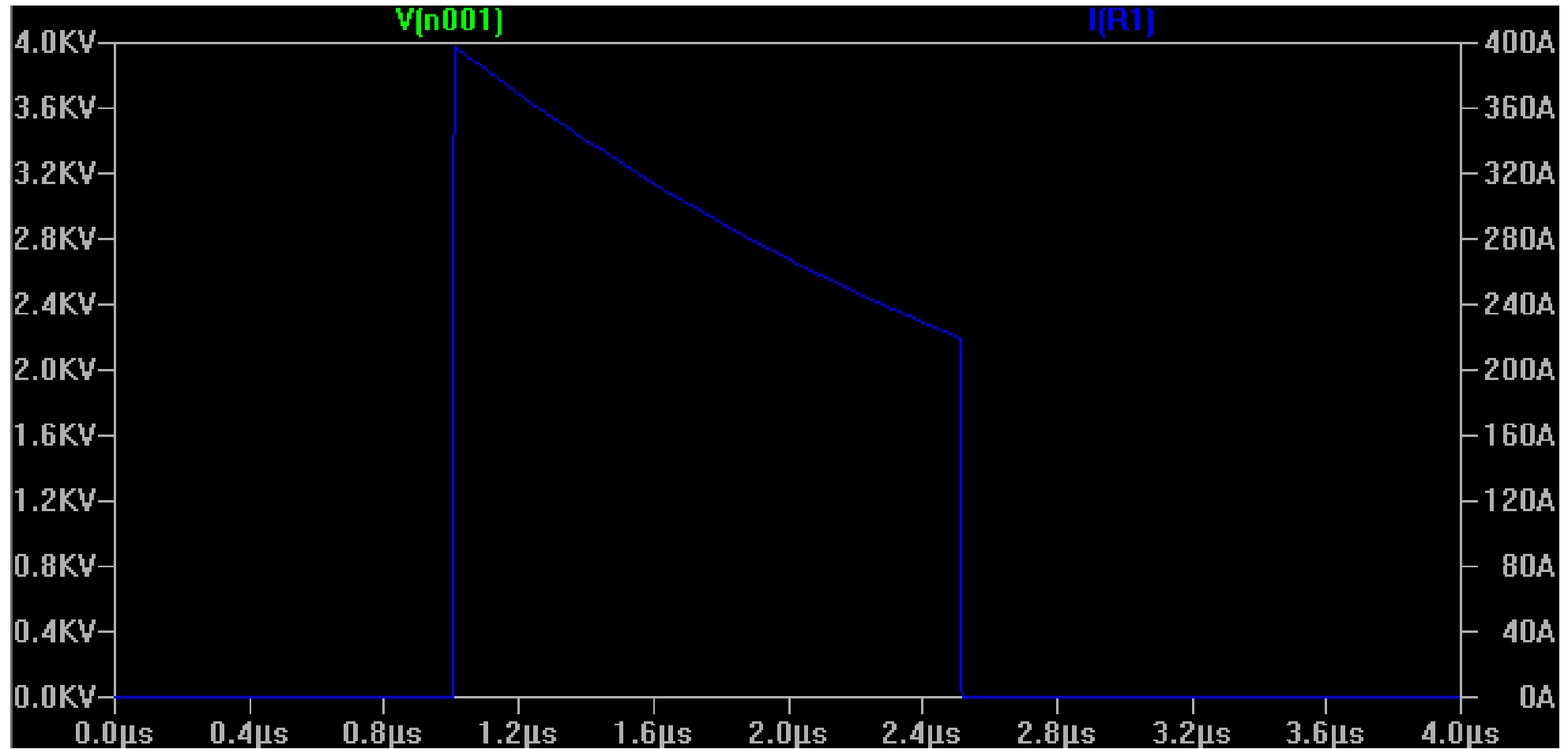
# Marx-parasitics

- Voltage instantly rises to 4kV, then has an RC decay until the cells turn off


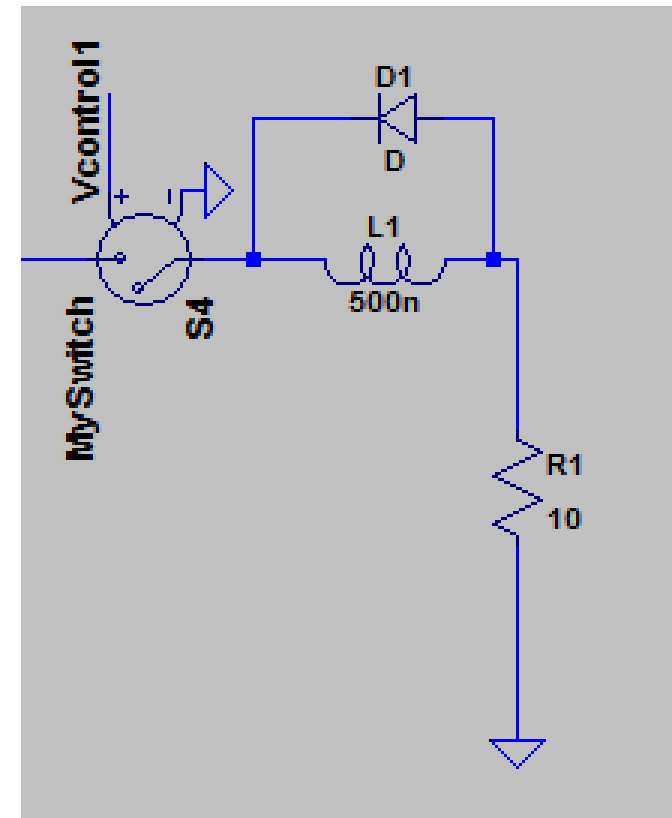
# Marx-parasitics


- Add a 500 nH inductance to the load
  - This could simulate parasitic inductance or intentionally added inductance.
- Free-wheeling diode conducts the current during Marx turn-off
  - Without, there would be a large voltage spike from the inductance





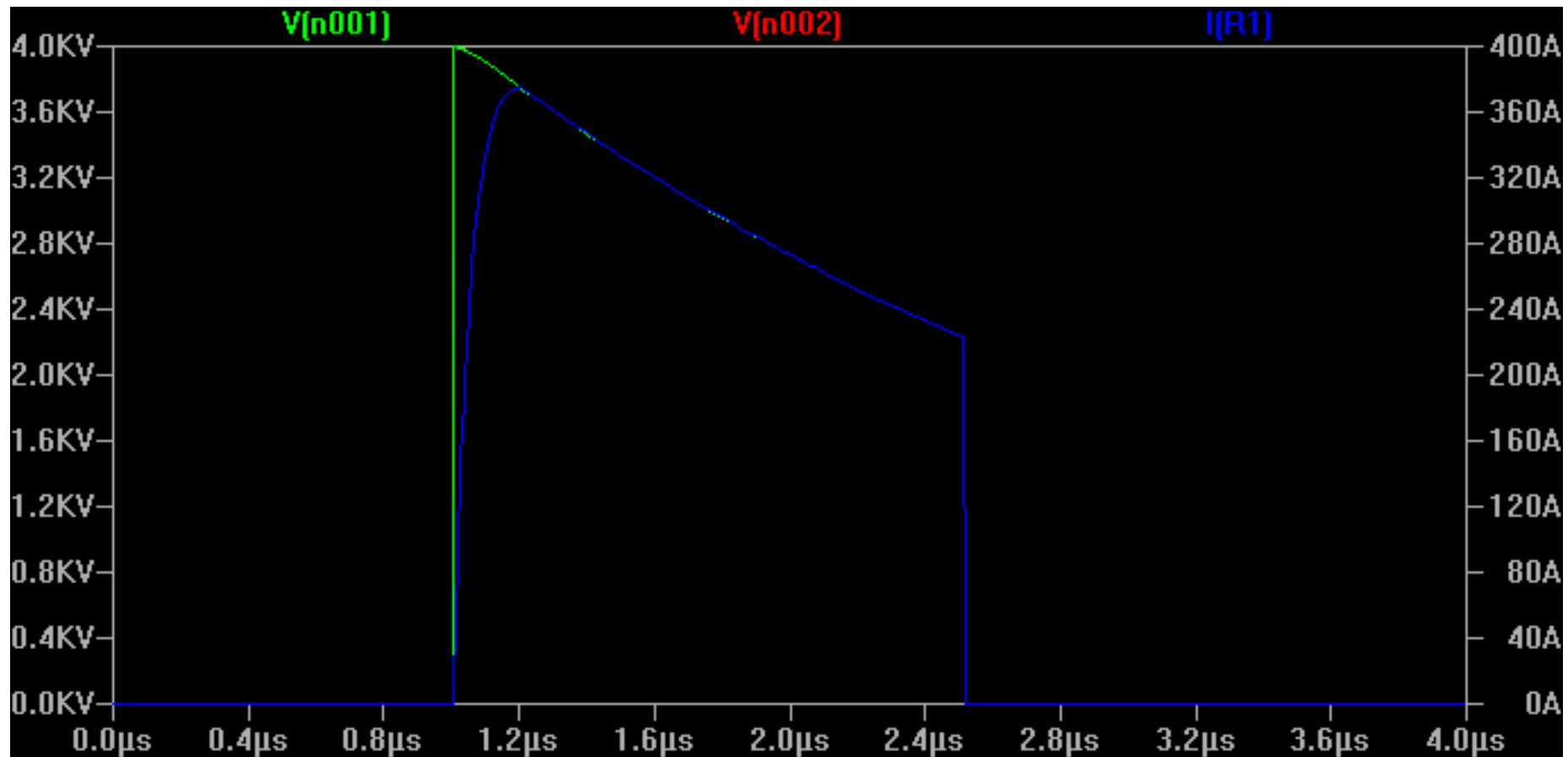
# Marx-parasitics

- L/R risetime added to rising front of current waveform.



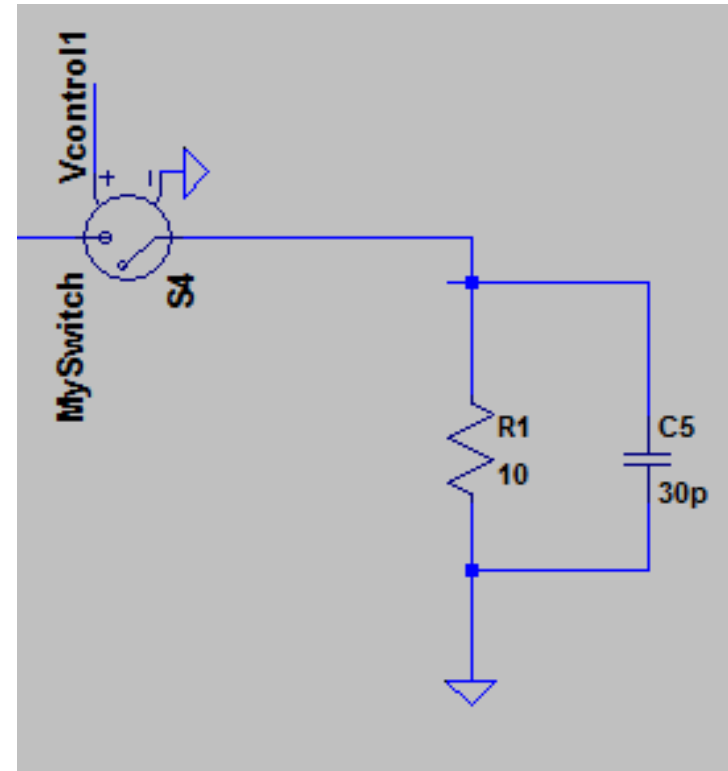
# Marx-parasitics

- Add a 30 pF capacitance in parallel with the load to simulate parasitic capacitance.


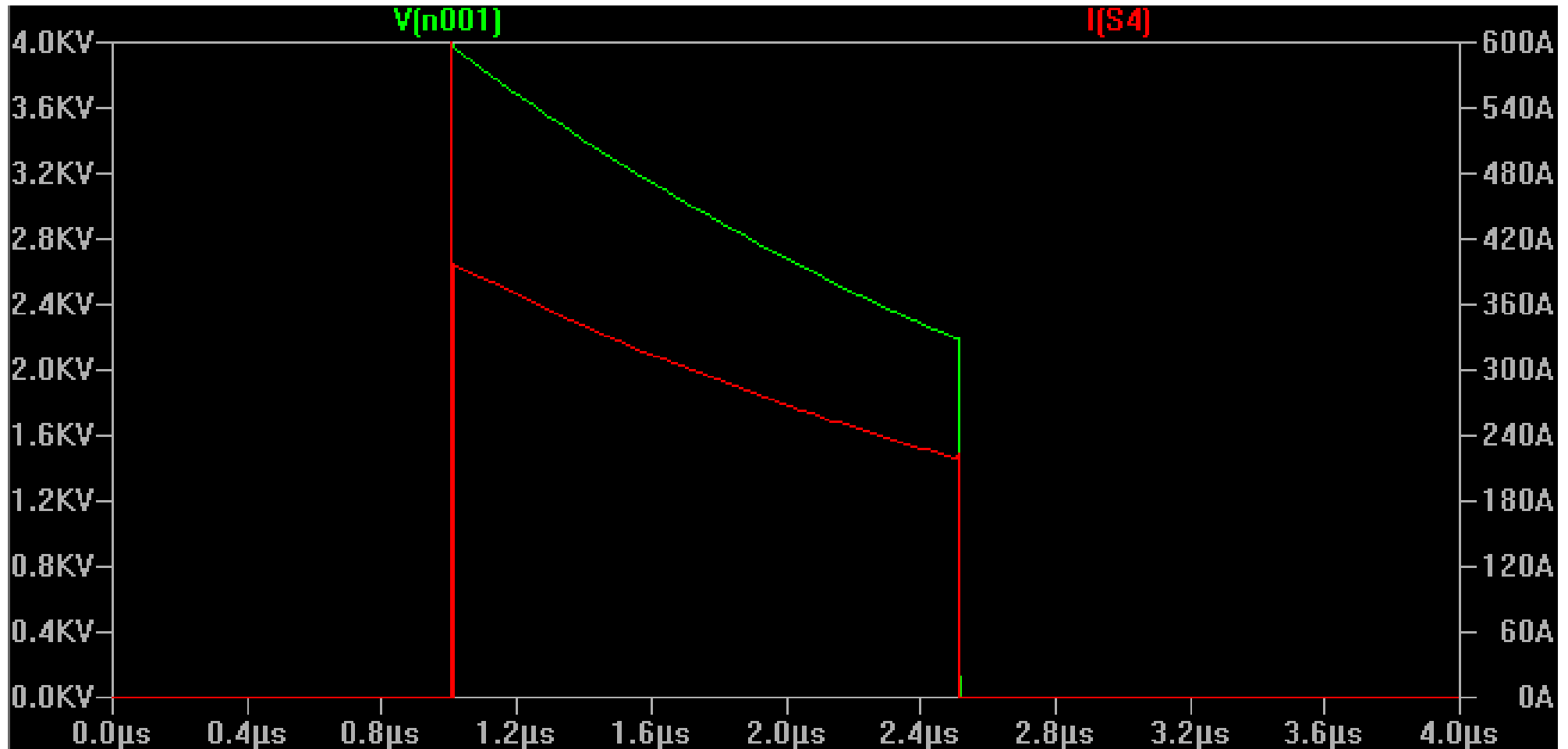
# Marx-parasitics

- Current spike as parasitic capacitance charges.



# Desired Characteristics of Next-Generation Modulators

Low Cost	Easily Maintained	High Availability	Superior Pulse Quality
Efficient operation	Simple construction	High mean time between failures	Pulse to pulse repeatability
Commoditized components from multiple vendors	Easy-to-get-to parts	Low mean time to repair	Operation into multiple impedance loads
Low fabrication costs	Simple safety procedures	Redundant architecture	Exceptional flat-top



# Desired Characteristics of Next-Generation Modulators

How does a Marx Modulator Achieve these characteristics?

Low Cost	Easily Maintained	High Availability	Superior Pulse Quality
<i>Modularity</i>			
<i>Low-Voltage Sub-Units</i>			
<i>Electrostatic Adding</i>			
<i>Independent Module Control</i>			



# Desired Characteristics of Next-Generation Modulators

- Modularity
  - Building blocks can be arranged in different configurations for different applications
  - Many inexpensive components
- Electrostatic Adding
  - Pulse transformer not necessary
- Independent Module Control
  - Reconfiguration possible
- Low-Voltage Sub-Units
  - Conventional power electronic converter techniques can be employed***
  - Commoditized components***




# Solid State Marx

- Use as a voltage multiplier to array solid state switches to klystron voltage requirements
  - Output  $\sim 0.1$  MV
  - Cells  $\sim$  few kV
  - Square output waveform
    - Hard switch (close/open) topology
    - Controlled switching of each cell
  - High average power
  - High PRF ( $> \text{Hz}$ )
  - Long life
- Solid state charging/isolation elements
  - Low loss
  - Minimize recharge time




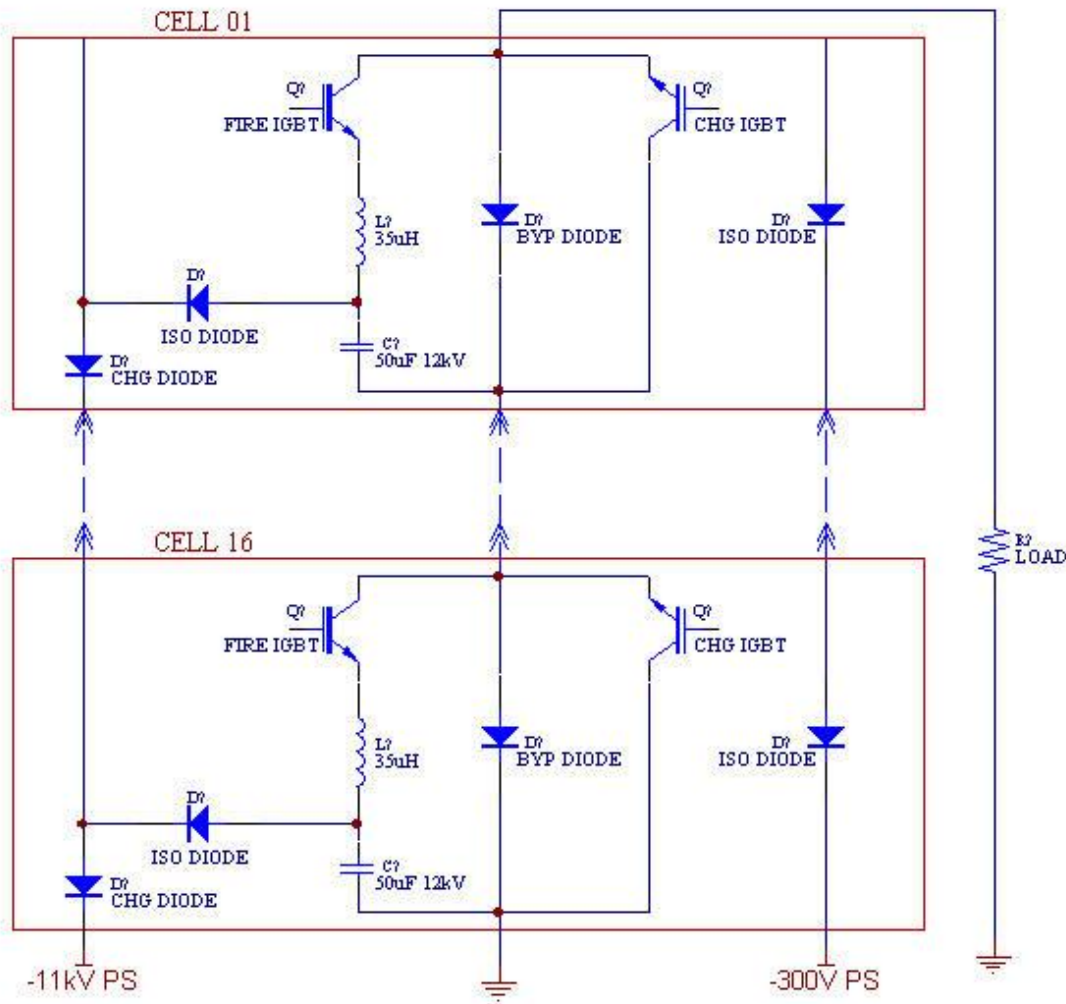
# Simplified Schematic of ILC-Marx P1-Prototype



- 11kV per Cell
- 16 Cells
  - 11 prompt cells → 120 kV
  - 5 delay cells, compensates capacitor droop
- Cell High Voltage Switches
  - Array of 4.5kV, 60A IGBTs 3 parallel X 5 series
  - Fire switches erect Marx
  - Charge switches provide current return path for main charging supply (-11 kV) and auxiliary power (-300 V)
- Diode Strings Provide Isolation Between Cells When Marx Erects
  - 18 series 1200 V, 60A, Ultrafast Soft Recovery Type
  - Parallel Resistors and MOVs to balance & protect against over-voltage
- Inductors Limit Fault  $di/dt$




# P1-Marx Voltage Regulation

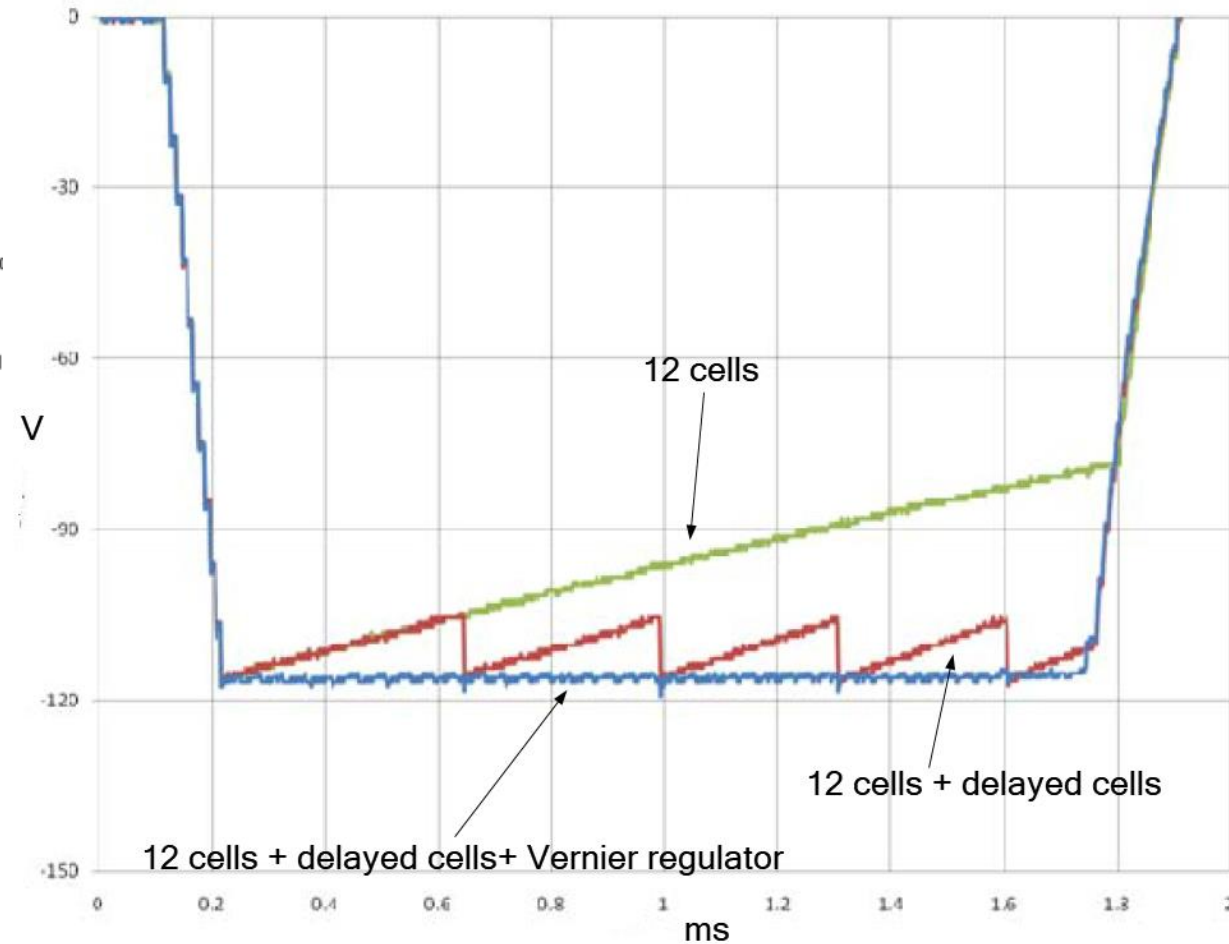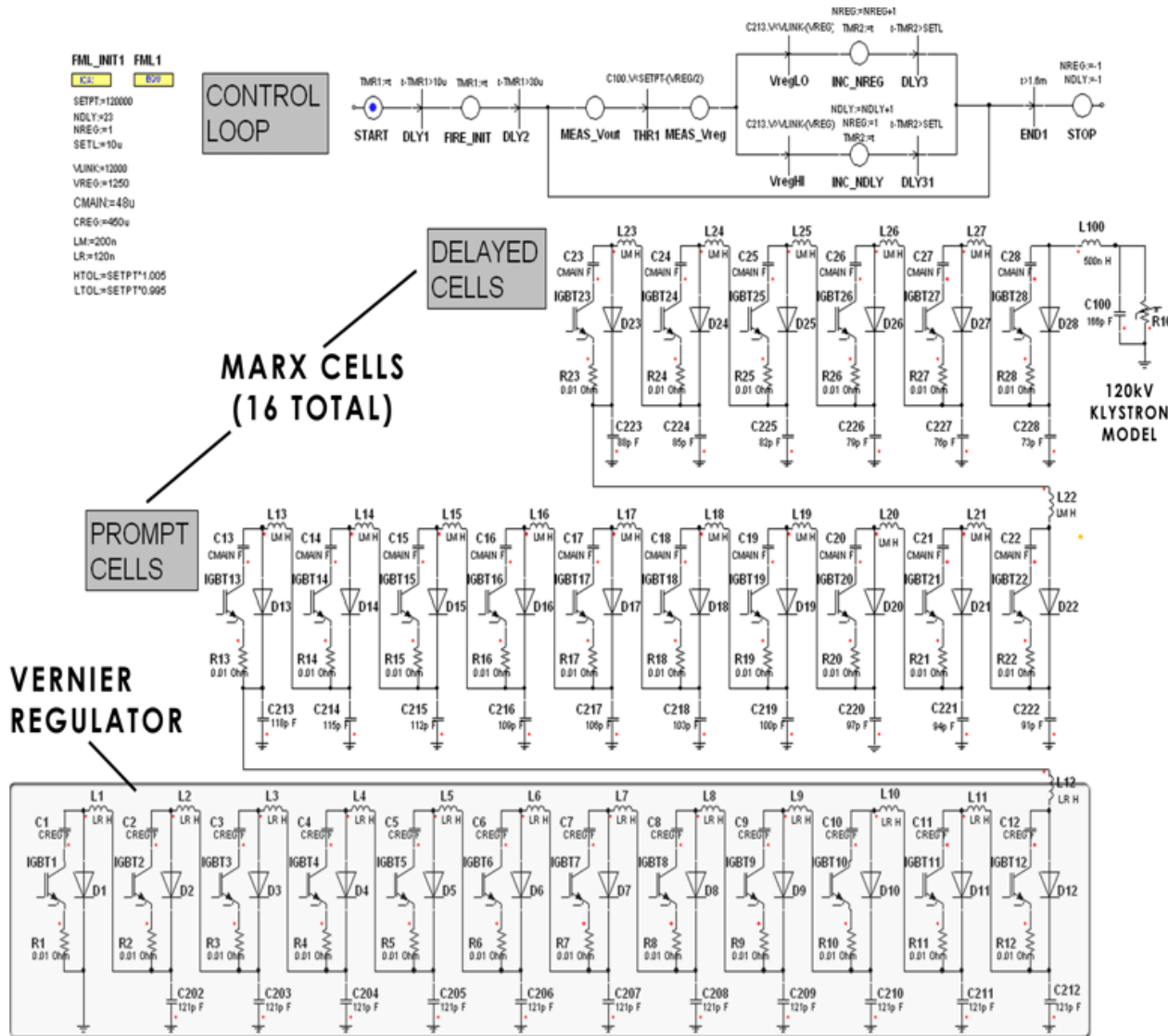

# P1-Marx Installed in “Sealed” Enclosure





# P1-Marx Cell Front & Rear Views

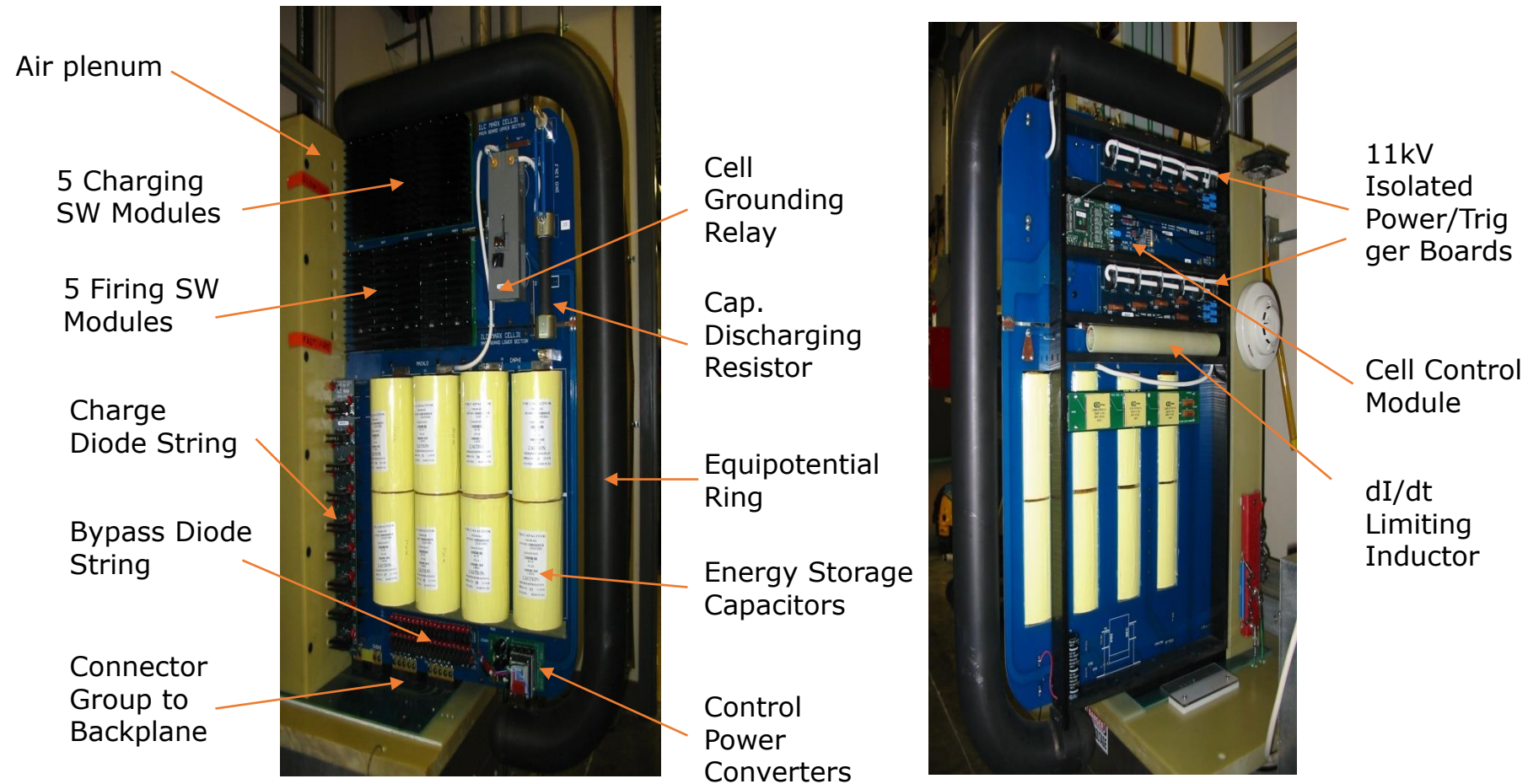





# The SLAC P2 Marx

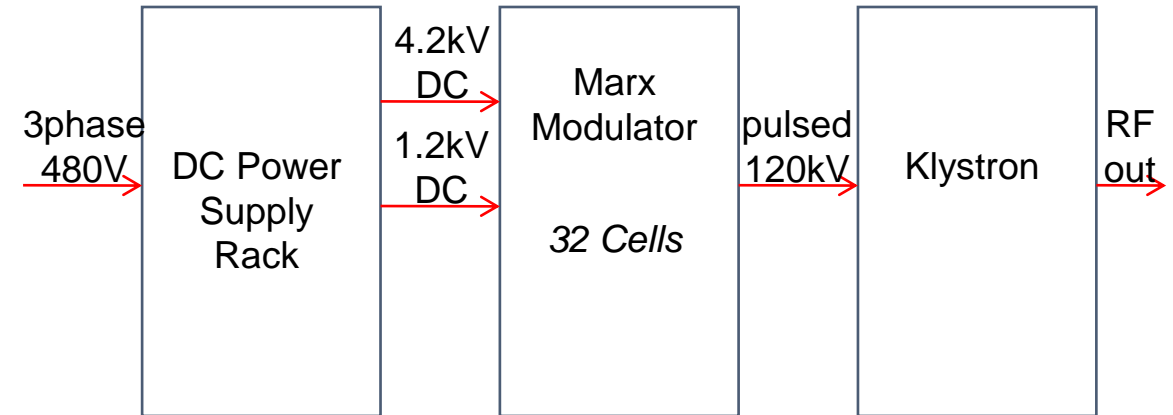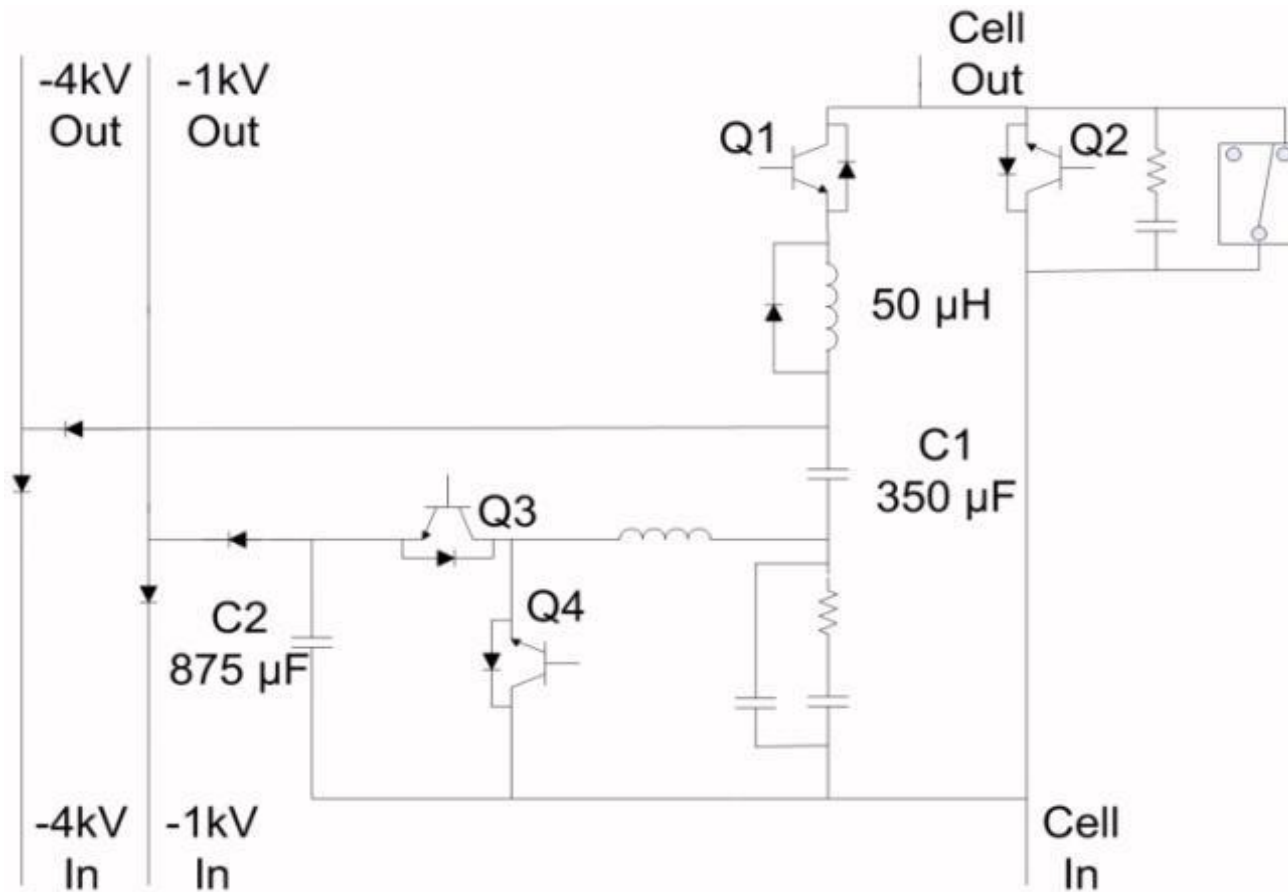


- Each Marx cell produces a flat-top: a “buck” converter is in series with the main cell capacitor
- The modulator regulation is closed-loop
- N+2 redundancy

# Buck Regulator

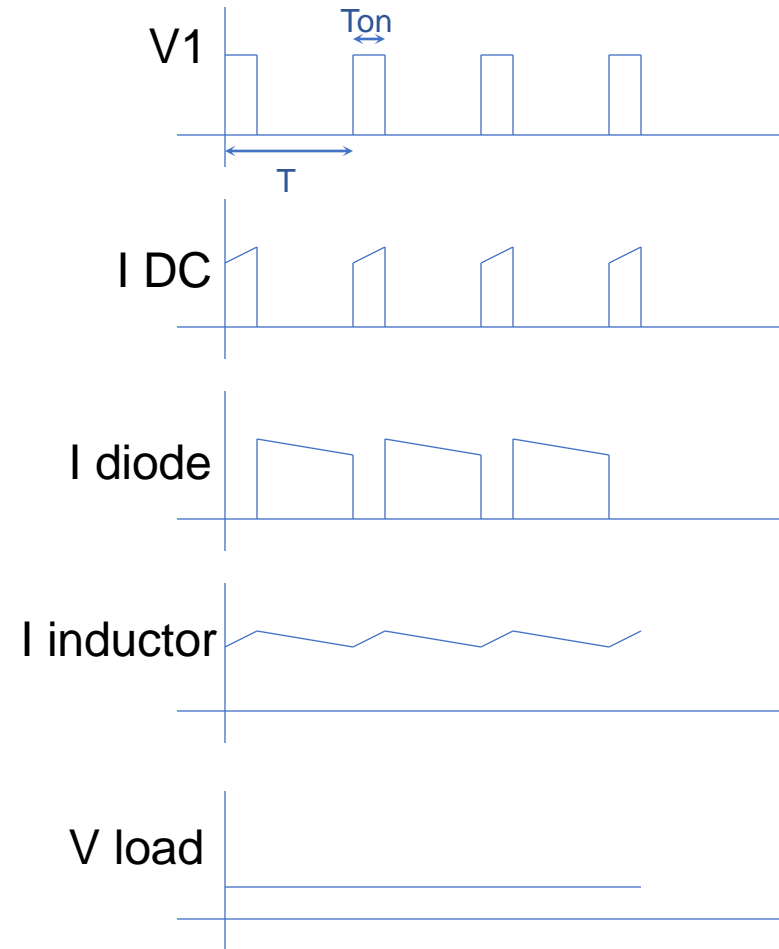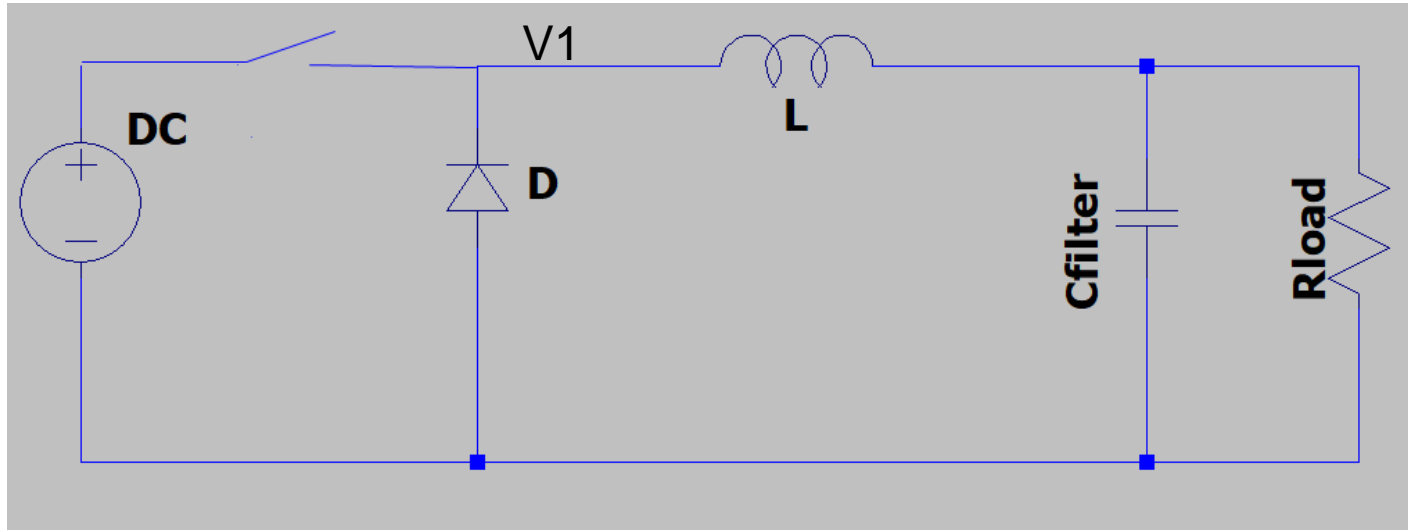

$$V_{\text{load}} = T_{\text{on}}/T * V_{\text{dc}}$$

# SLAC P2 Marx Photographs



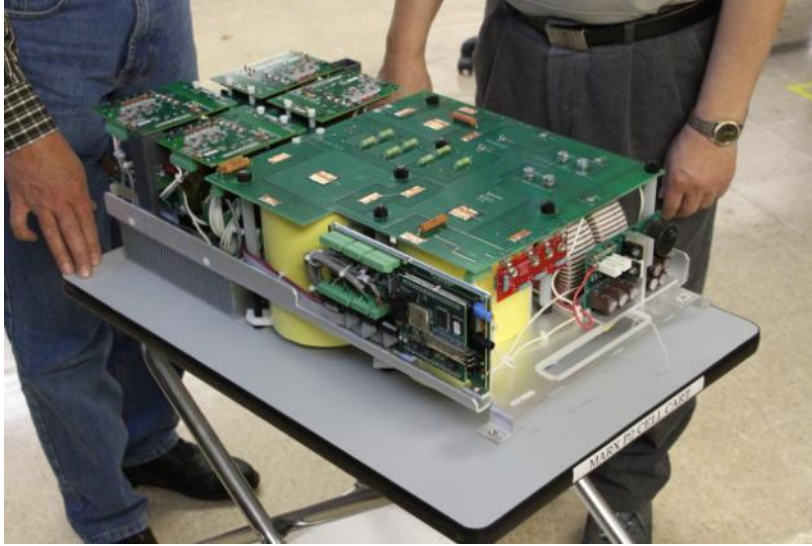


Pulsed Power Engineering  
Winter 2022





**U.S. Particle Accelerator School**  
Education in Beam Physics and Accelerator Technology

# SLAC P2 Marx Cell Schematic

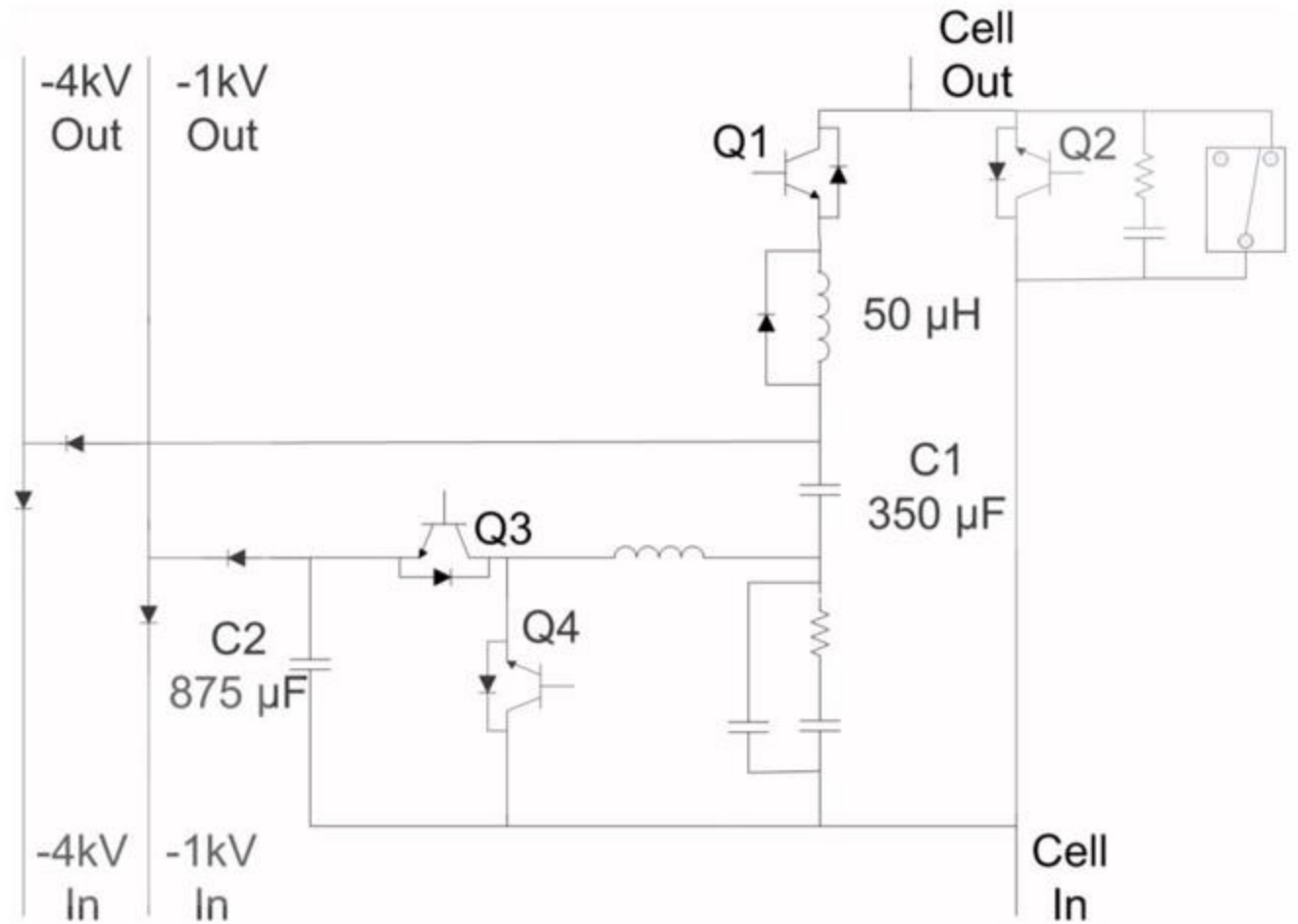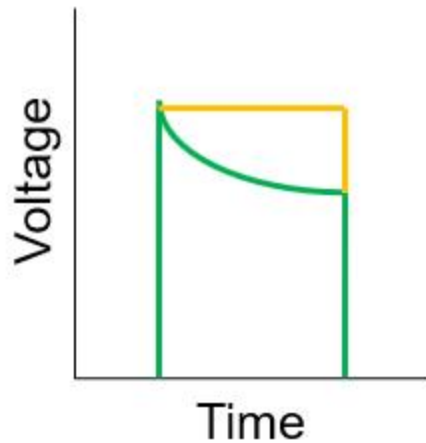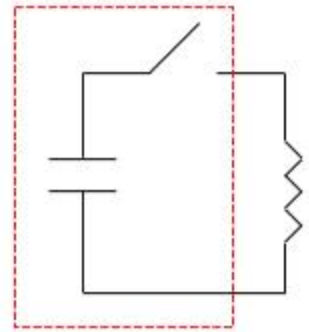


# Correction Scheme

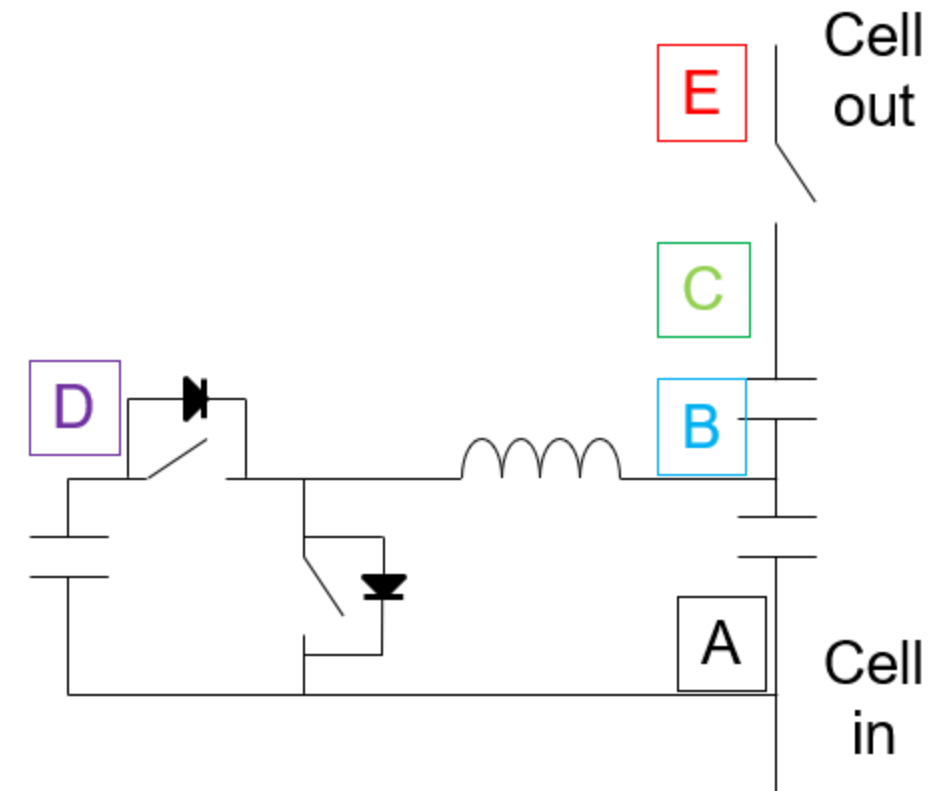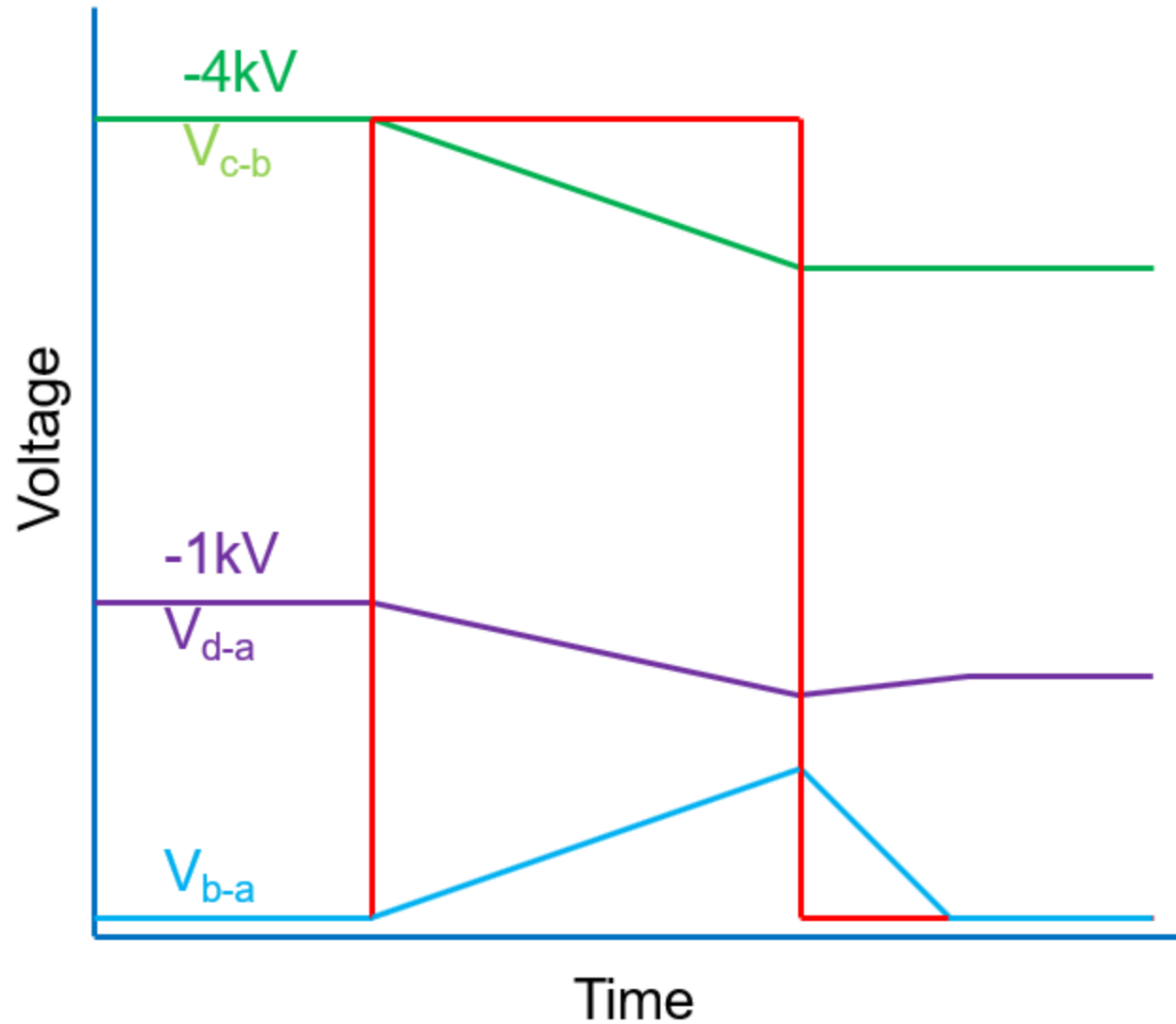

(negative bus voltage)



# Correction Scheme

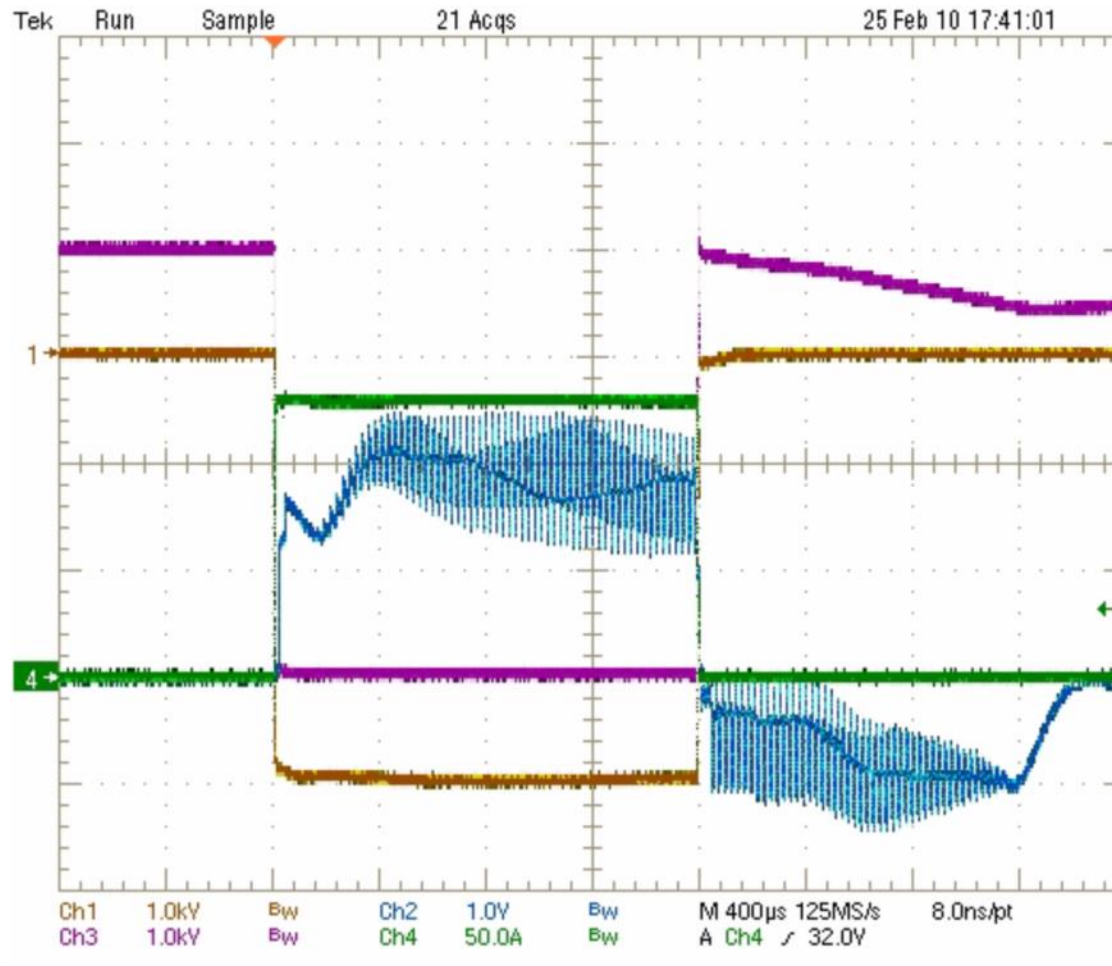


Cell Output Current

Cell Output Voltage



Main IGBT  $V_{ce}$

PWM Inductor Current

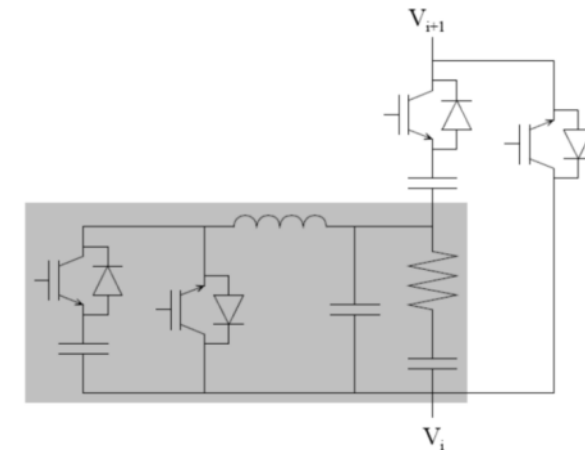
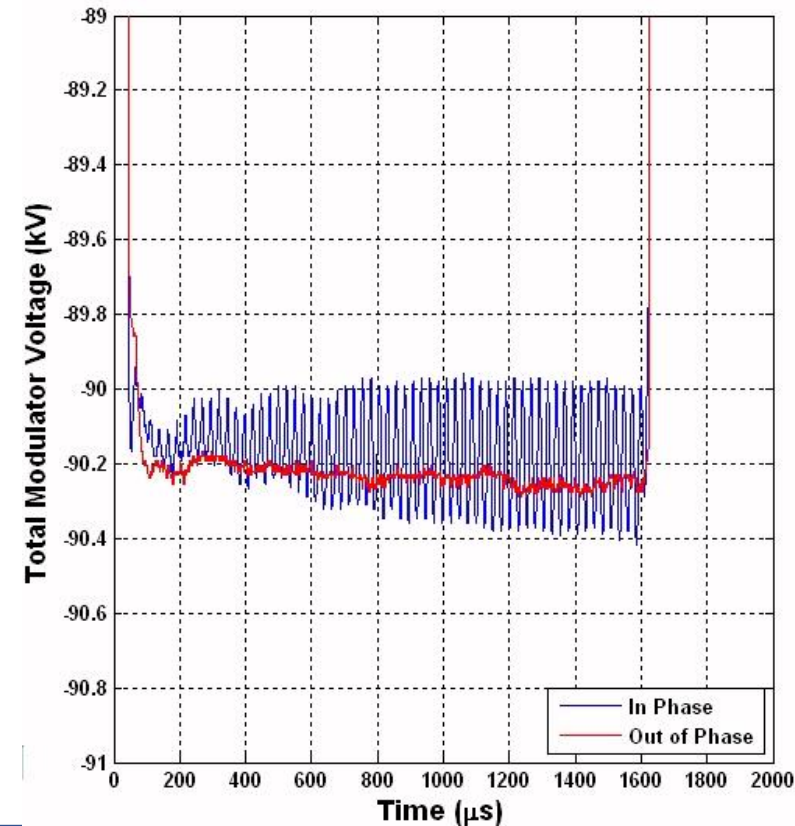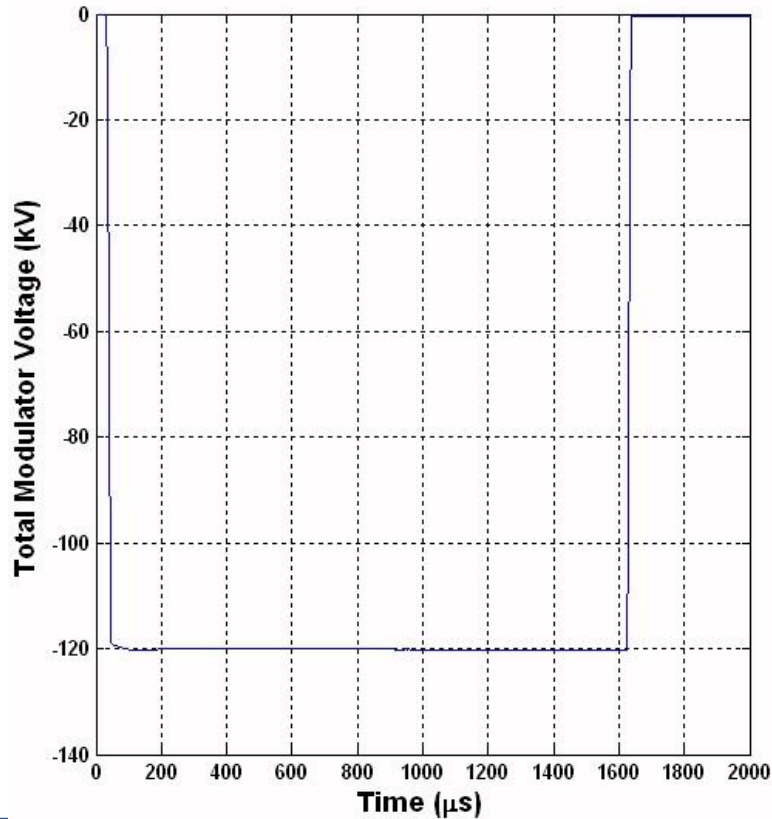
# SLAC P2 Marx Performance

- Marx rise and fall times are  $\sim 10 \mu\text{s}$
- A flat top has been demonstrated  $\rightarrow \pm 0.05\%$  over 1.6ms




# SLAC P2 Marx: Simple Maintenance




- A single cell can be changed in 2 minutes
- Maintenance is “back at the shop” rather than at the modulator -> low MTTR

# SLAC P2 Marx Control System

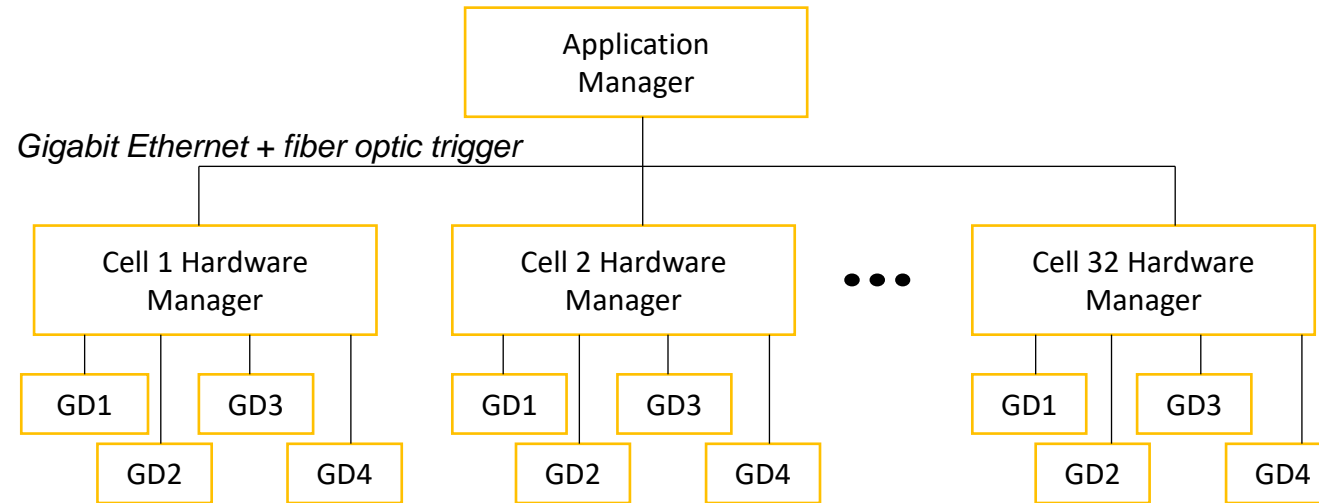


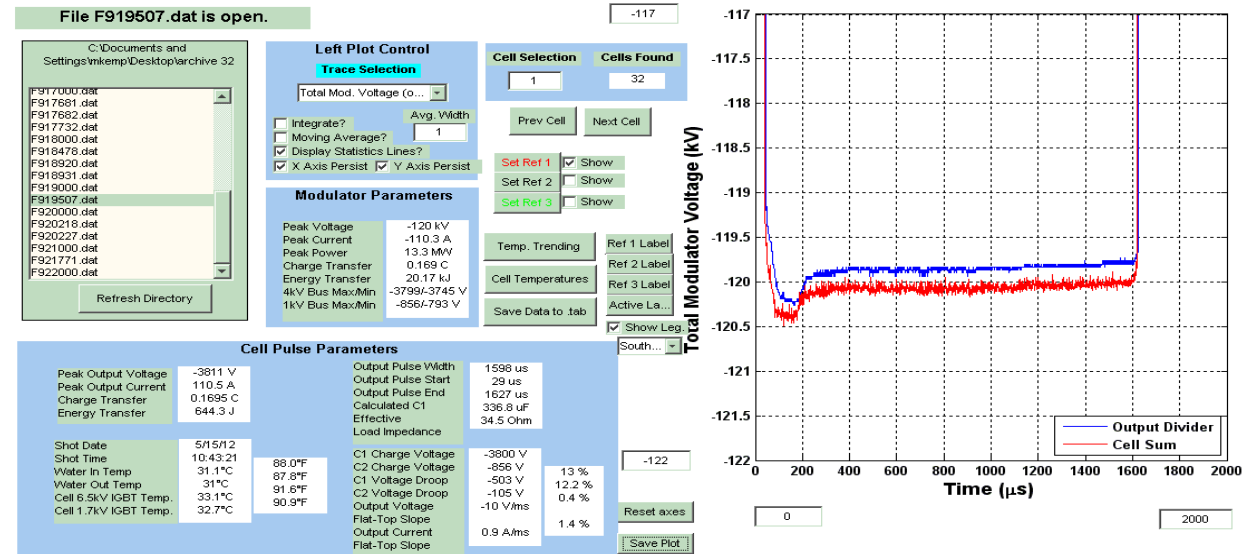- 256, 12-bit, 1 MS/s, 2.1ms-long waveforms are captured each shot







# Some Embodiments of the Technology

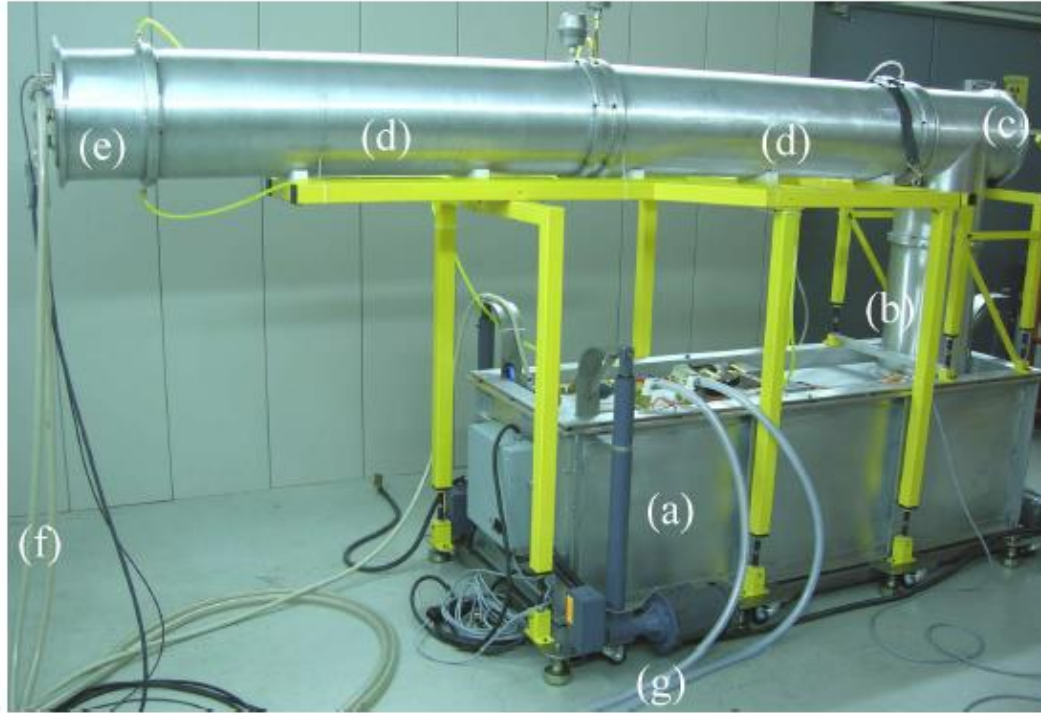


## NRL Marx Modulator for KrF Laser

• -200 kV, -5 kA, 300 ns, 10 Hz pulses

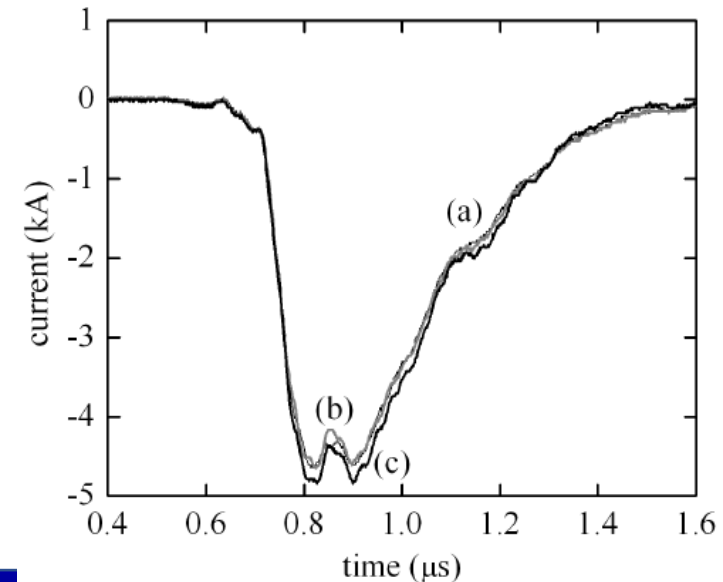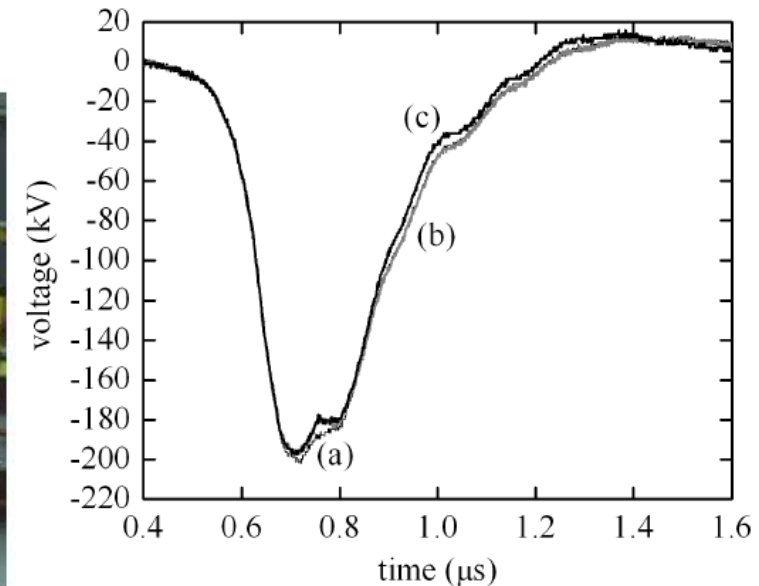F. Hegeler, et al., "A Durable Gigawatt Class Solid State Pulsed Power System, Trans. Plasma Sci. 2011.



# 201 MHz Linac Triode

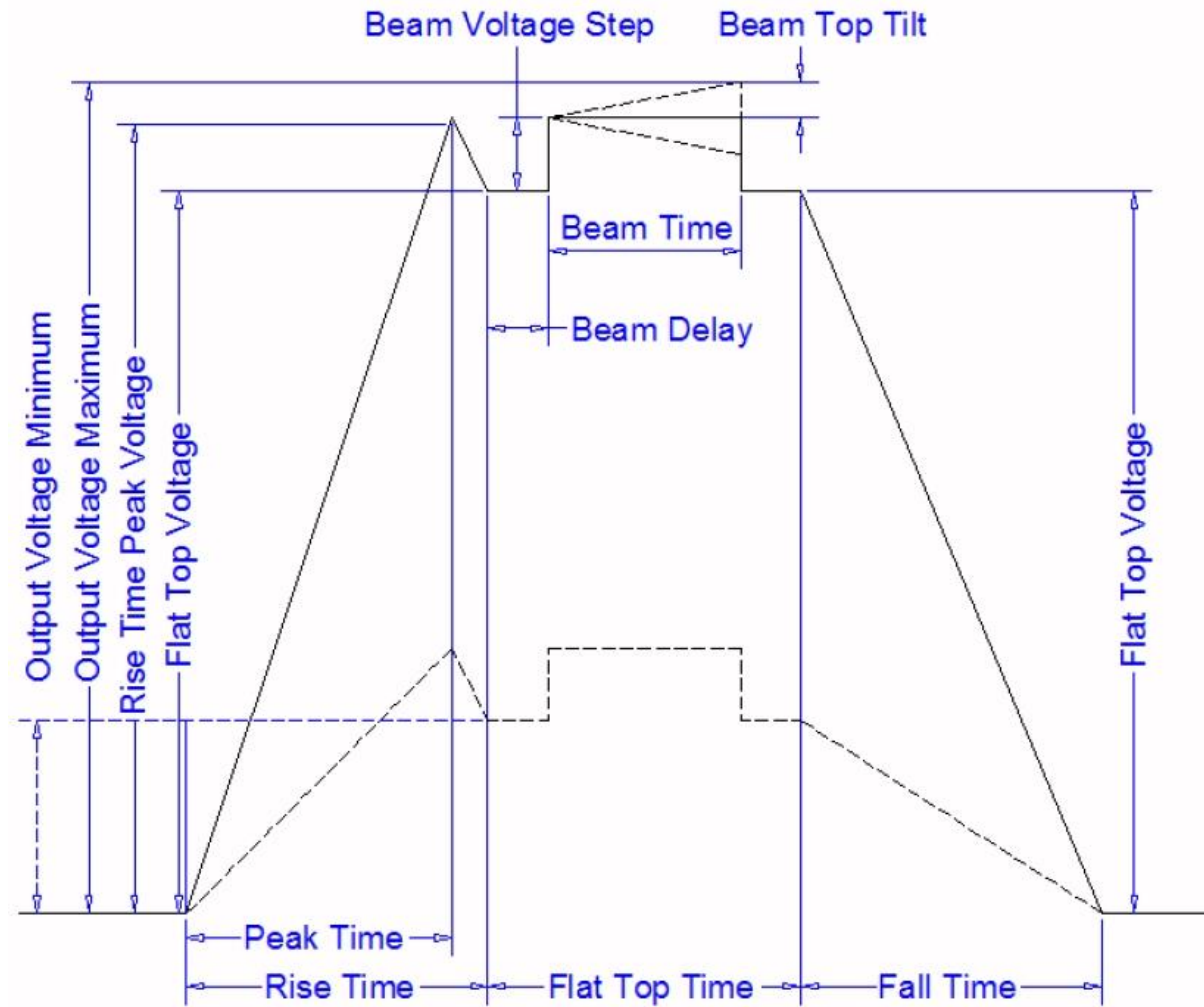

# Fermi Designed/Built Modulator For This Load [1]

## FNAL Linac Marx Topology

### 41 Main Marx Cells (900 V)



- Create the rising and falling edges
- Limits cavity reflected power back to tube

### 12 Pulse Width Modulation Cells (900 V)

- Interleaved & filtered regulator w/ 7 kV range
- Flatten capacitive droop & regulate flattop voltage via feedback & learning algorithms

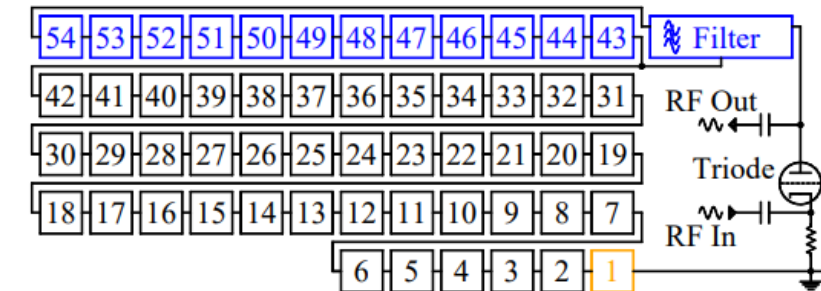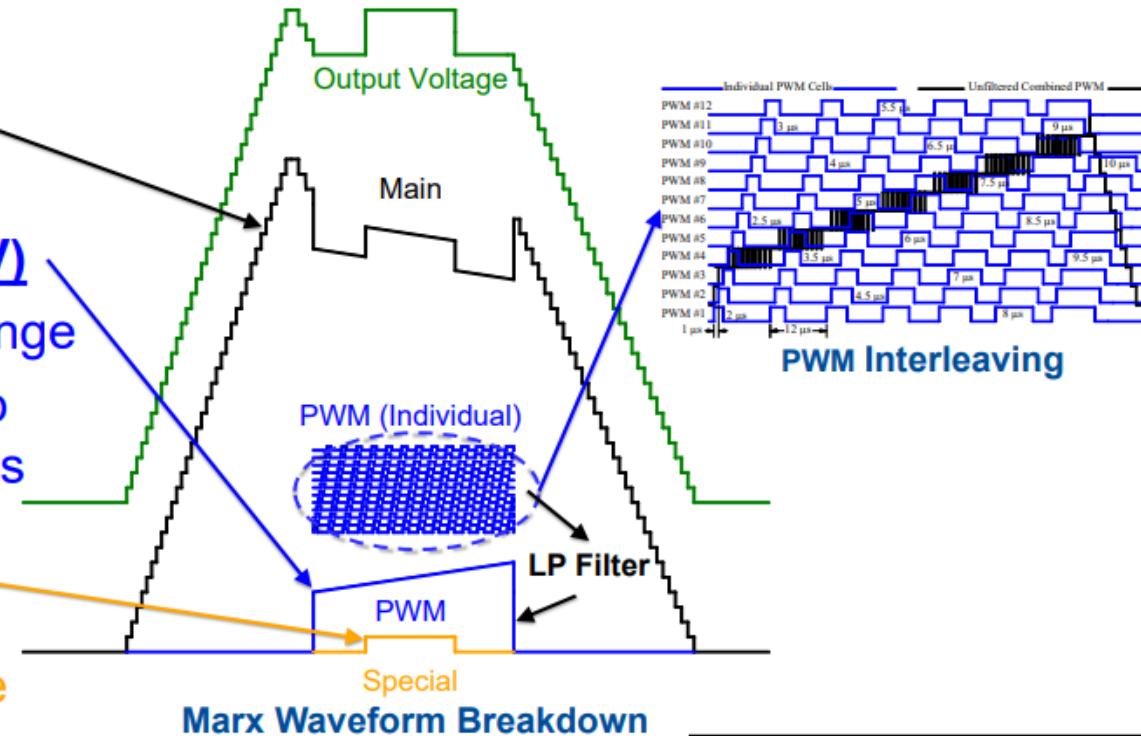
### 1 Special Cell (0 to 900 V)

- Independently adjustable charging PS
- Enables fractional beam voltage step size



[1] Development of a Marx Modulator for FNAL Linac Trevor A. Butler, F. G. Garcia, M. R. Kufer, K. S. Martin, H. Pfeffer, FNAL, Batavia, IL 60510, USA . Poster. NAPAC 2019.
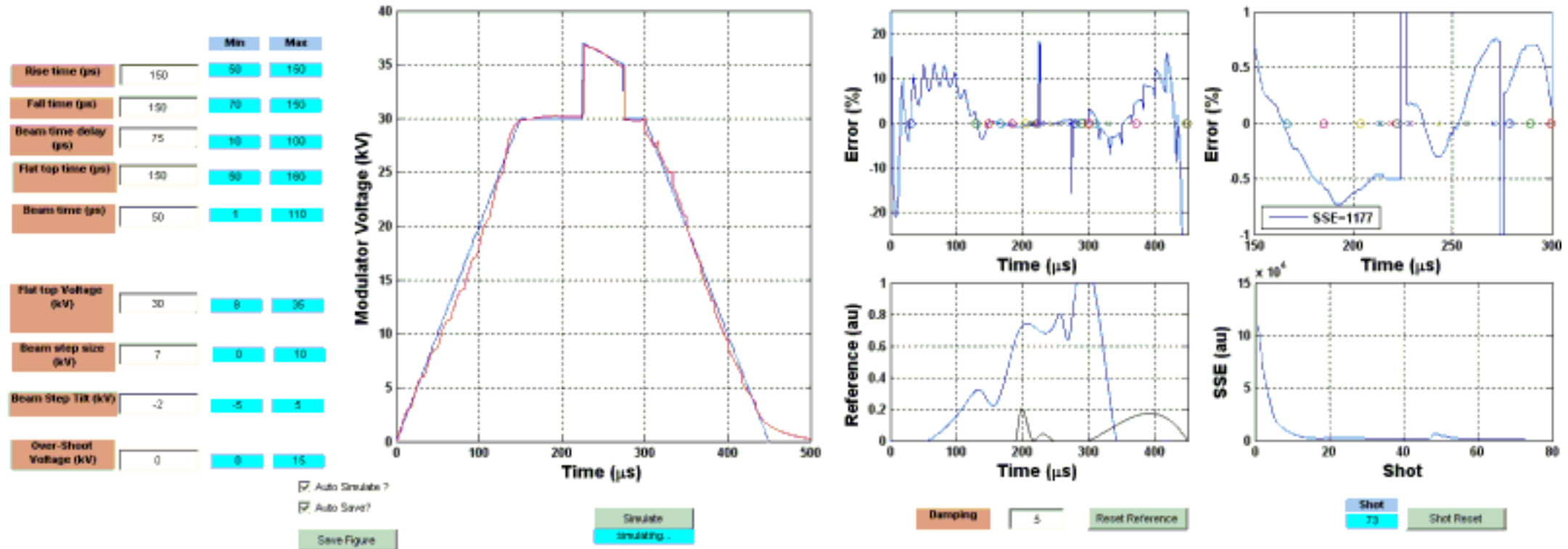
# 201 MHz Linac Triode Modulator Early Paper Study (Feed Forward)





# Scaling of the Technology to Emerging Applications

- The ILC P2 Marx building block has:
  - A maximum voltage (4kV)
  - A maximum peak current (200A)
    - Can increase by changing switches
  - A maximum average power
    - Can increase by changing cooling
  - A maximum energy transfer per pulse
    - Can increase by increasing cell capacitance

